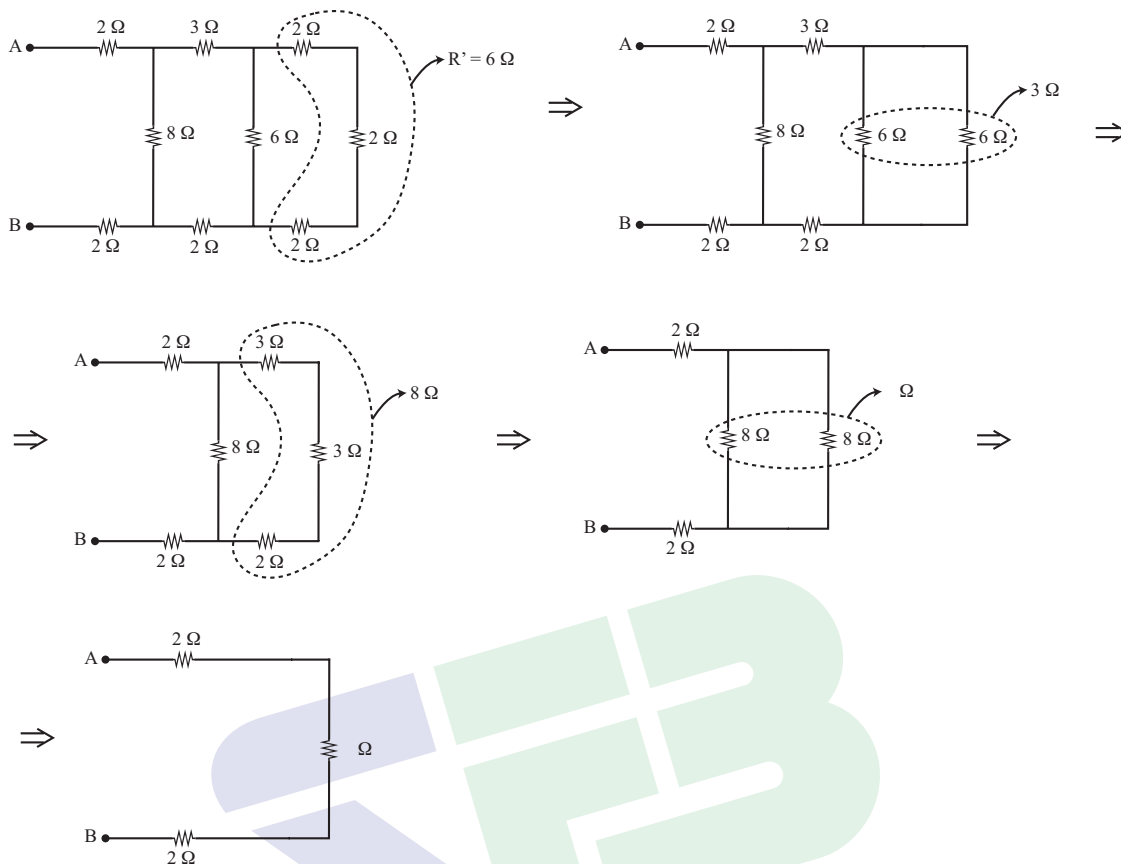




01.




$$R_{eq} = 2 + 4 + 2$$

$$R_{eq} = 8 \Omega$$

**Resposta: C**

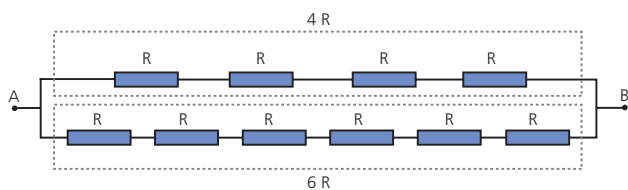02. Dados:  $R = 20 \Omega$ ;  $U = 120 \text{ V}$ .  
O arranjo dado equivale ao esquema abaixo:





A resistência equivalente é:

$$R_{eq} = \frac{6R \cdot 4R}{6R + 4R} = \frac{24R^2}{10R} \Rightarrow R_{eq} = 2,4R = 2,4 \cdot 20 \Rightarrow$$

$$R_{eq} = 48 \Omega$$

**Resposta: E**

03.

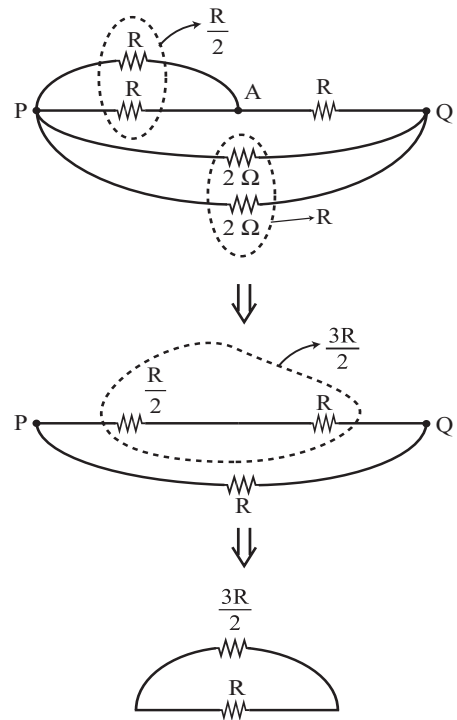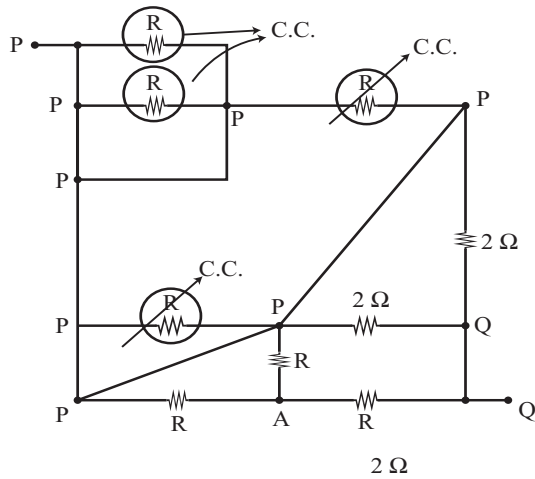


$$R_{eq} = \frac{\frac{3R}{2} \cdot R}{\frac{3R}{2} + R} = \frac{3R^2}{5R}$$

$$R_{eq} = \frac{3R}{5} \Rightarrow R_{eq} = \frac{3 \cdot 5}{5} \Rightarrow \boxed{R_{eq} = 3 \Omega}$$

Resposta: C


04. Para a associação abaixo:

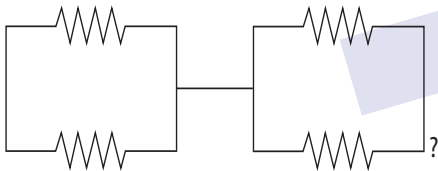

$$R_{eq} = \frac{R}{2} + \frac{R}{2} = \frac{2R}{2} \Rightarrow \boxed{R_{eq} = R}$$

Resposta: D

05.

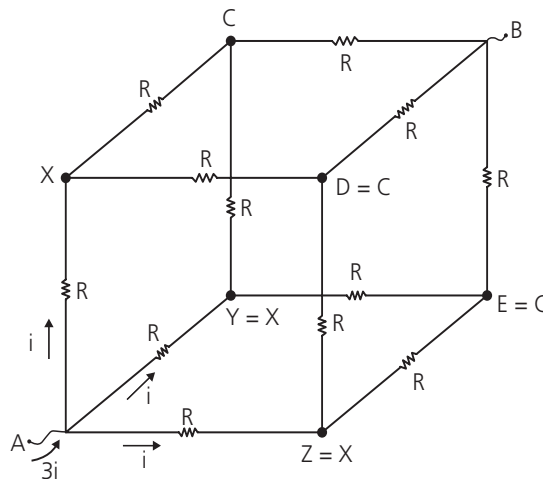

## Resolução – Física II

Supondo que uma corrente de  $3i$  entre no ponto A, temos:

$$V_A - V_Z = R \cdot i$$


$$V_A - V_Y = R \cdot i$$

$$V_A - V_X = R \cdot i$$

$$\text{Logo: } V_A - V_Z = V_A - V_Y = V_A - V_X \Rightarrow V_Z = V_Y = V_X$$

Por Analogia:

$$V_C = V_D = V_E$$

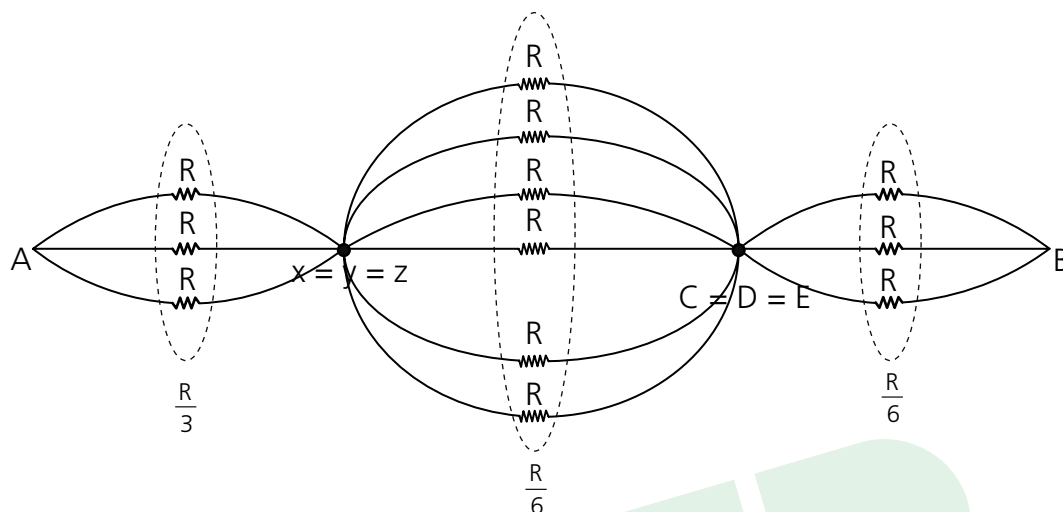

$$R_{eq} = \frac{R}{3} + \frac{R}{6} + \frac{R}{3}$$

$$R_{eq} = \frac{5R}{6} \Rightarrow R_{eq} = \frac{5 \cdot 6}{6} \Rightarrow \boxed{R_{eq} = 5 \Omega}$$

**Resposta: B**